
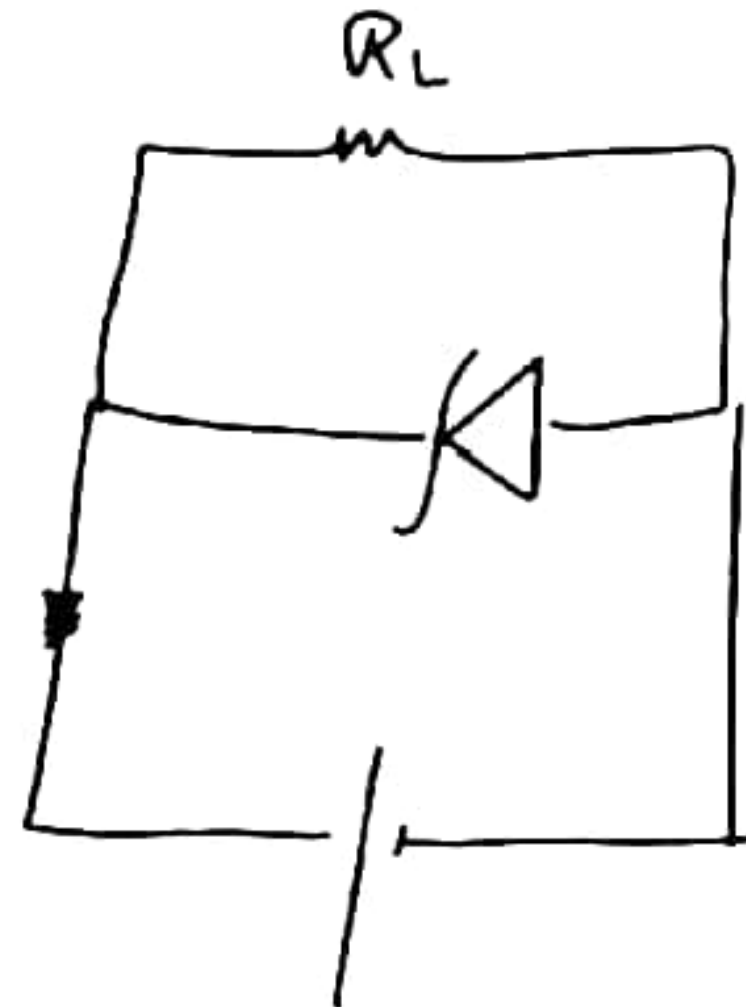


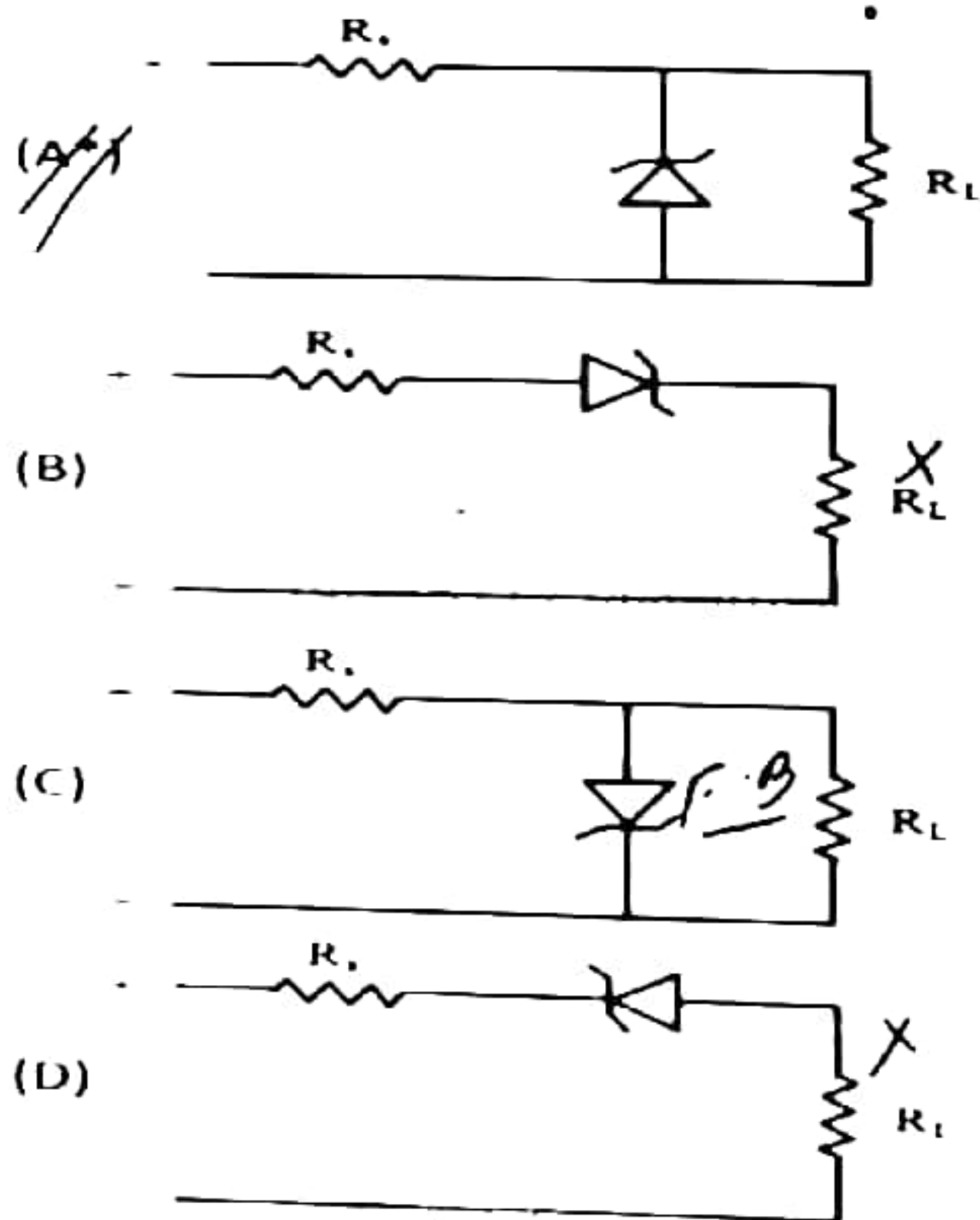1.

A zener diode is to be used as a voltage regulator. Identify the correct set up



2.

**Statement 1** : Conductivity of semiconductors decreases with increase in temperature. *in correct*

**Statement 2** : More electron goes from valance band to conduction band with increase in temperature. *correct*

(A) Both Statement-1 and Statement-2 are true, and Statement-2 is the correct explanation of Statement1.


(B) Both Statement-1 and Statement-2 are true but Statement-2 is not the correct explanation of Statement-1.

(C) Statement-1 is true but Statement-2 is false.

☒ (D\*) Statement-1 is false but Statement-2 is true.

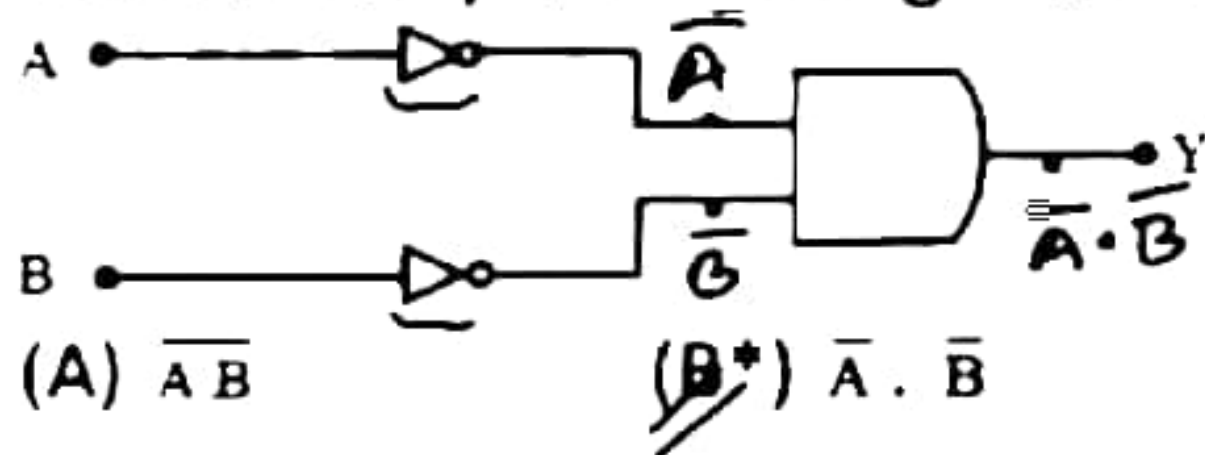
3.

What is out put Y of the gate circuit shown in figure?



4.


Following circuit is equivalent to -

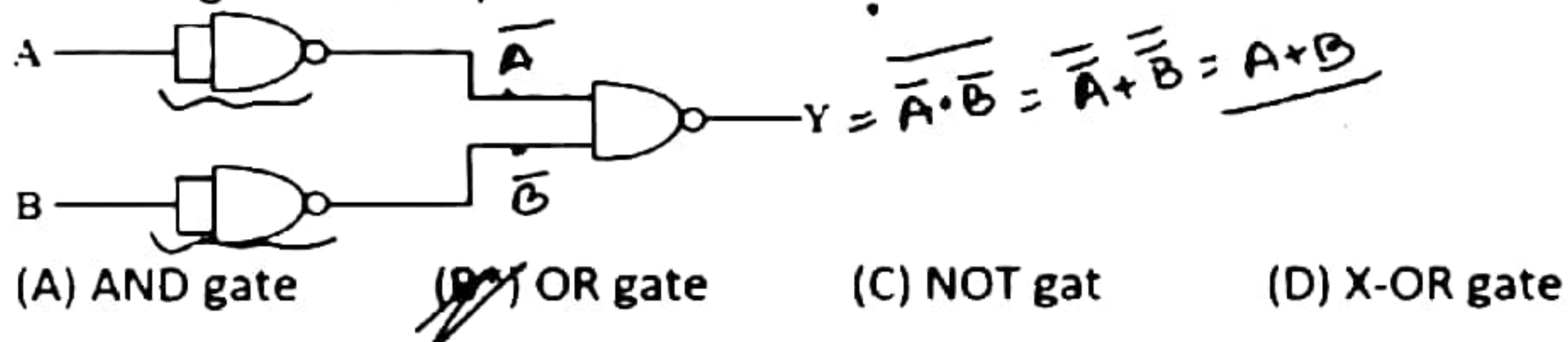

5.

Depletion layer in the p-n junction consists of -

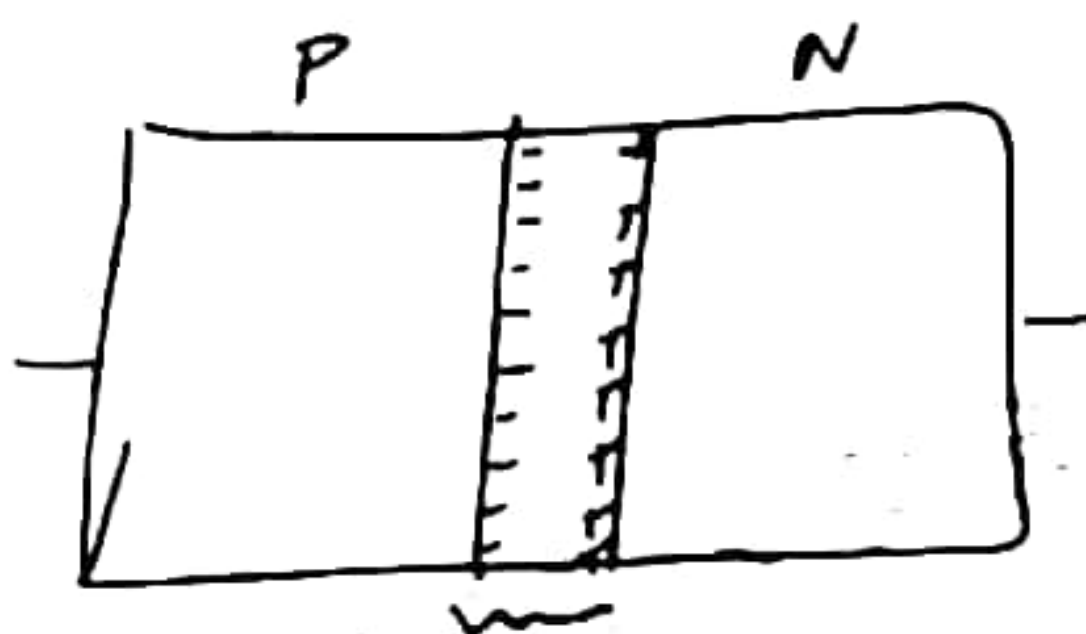- (A) electrons
- (B) holes
- ~~(C\*)~~ positive and negative ions fixed in their position
- (D) both electron and holes





6.

The depletion layer in silicon diode is  $1\mu\text{m}$  wide and the knee potential is  $0.6\text{ V}$ , then the electric field in the depletion layer will be -

- (A) Zero (B)  $0.6\text{Vm}^{-1}$  (C)  $6 \times 10^4\text{ V/m}$  ~~(D\*)~~  $6 \times 10^5\text{ V/m}$

$$d = 1\mu\text{m}$$


$$V_B = 0.6\text{ V}$$

$$E = \frac{V}{d} = \frac{0.6\text{ V}}{10^{-6}\text{ m}}$$

$$= 6 \times 10^5\text{ V/m}$$

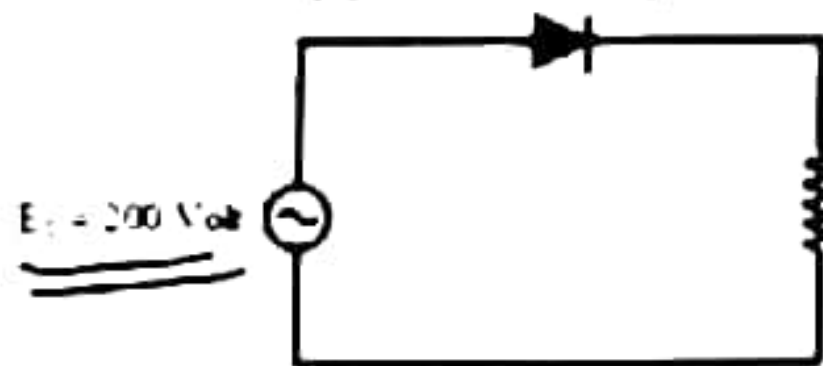7.

A sinusoidal voltage of peak value  $200\text{ volt}$  is connected to a diode and resistor  $R$  in the circuit shown so that half wave rectification occurs. If the forward resistance of the diode is negligible compared to  $R$  the rms voltage (in volt) across  $R$  is approximately -



$$V_{RMS} = \frac{V_0}{2} = \frac{200}{2} = 100\text{ V}$$

(A) 200


~~(B\*)~~ 100

(C)  $\frac{200}{\sqrt{2}}$

(D) 280

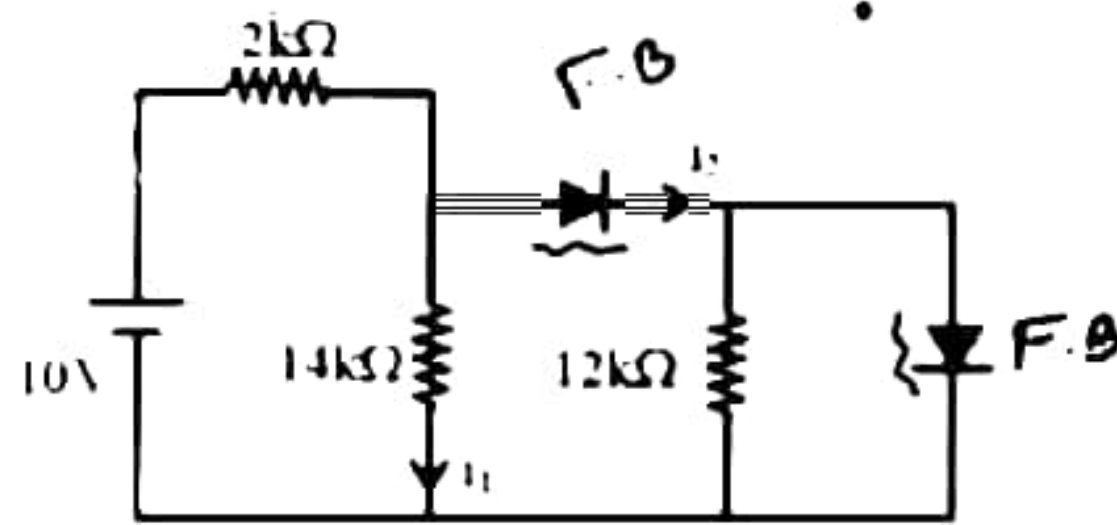8.

In the following circuit find  $i_1$  and  $i_2$  -




(A) 0,0

(B) 5 mA, 5 mA


(C) 5 mA, 0

~~(D) 0, 5 mA~~

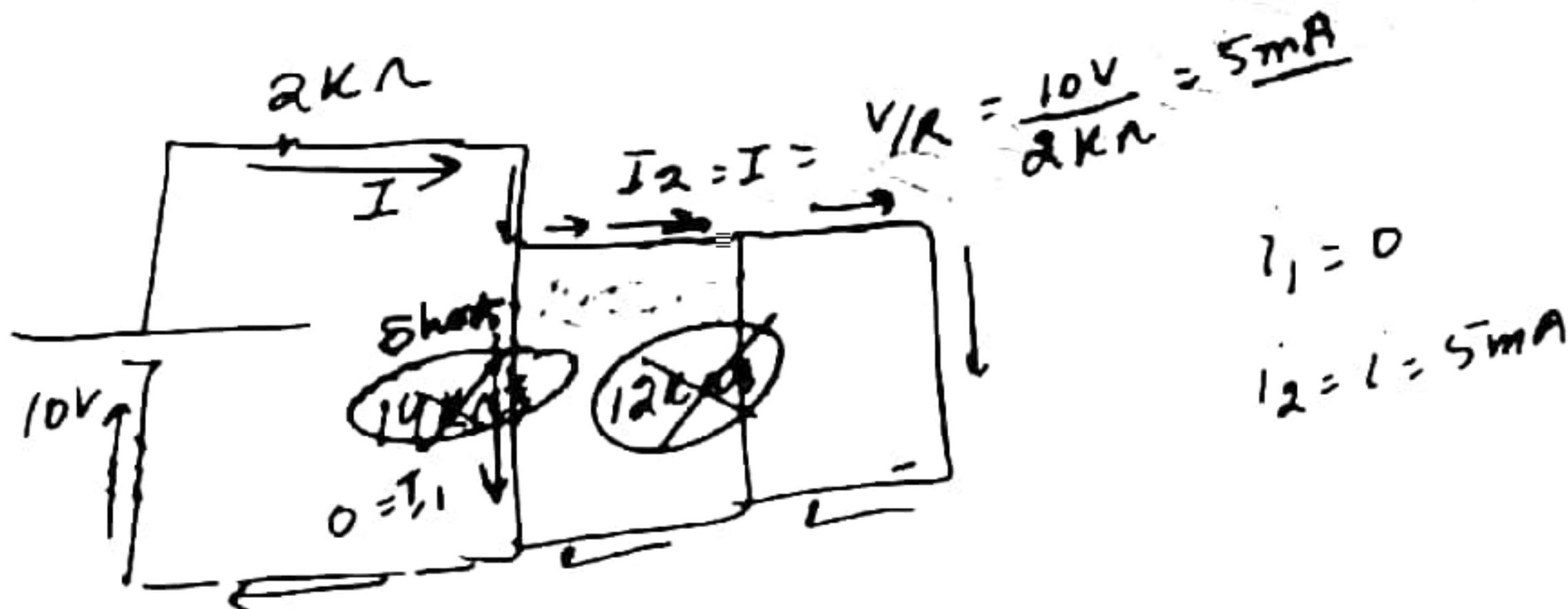

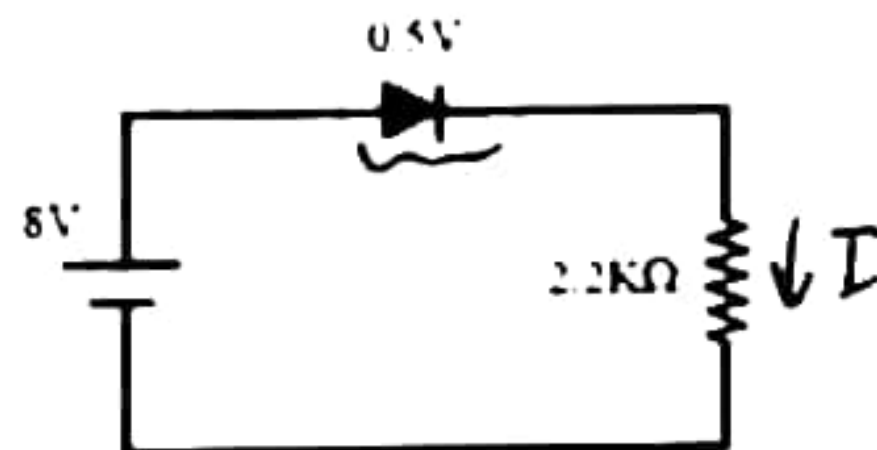9.

In the circuit, if the forward voltage drop for the diode is 0.5V, the current will be -



~~(A) 3.4 mA~~

(B) 2 mA

(C) 2.5 mA

(D) 3 mA

$$8 - 0.5 = I \times 2.2k\Omega$$


$$\frac{7.5V}{2.2k\Omega} = I$$

$$I = 3.4mA$$



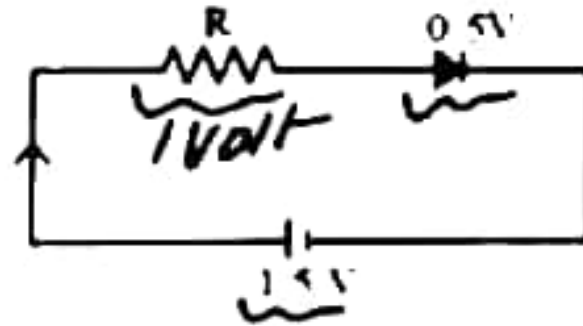10.

The diode used in the circuit shown in the figure has a constant voltage drop of 0.5 V at all currents and a maximum power rating of 100 milliwatts. What should be the value of the resistor R, connected in series with the diode for obtaining maximum current –



- (A) 1.5  $\Omega$       ~~(B) 5  $\Omega$~~       (C) 6.67  $\Omega$       (D) 200  $\Omega$

$$P_{max} = 100 \text{ mW} = V \cdot I$$


$$100 \text{ mW} = 0.5 I_{max}$$

$$I_{max} = 200 \text{ mA}$$

$$V = IR \quad R = \frac{V}{I} = \frac{1 \text{ Volt}}{200 \times 10^{-3}} = \underline{\underline{5 \Omega}}$$

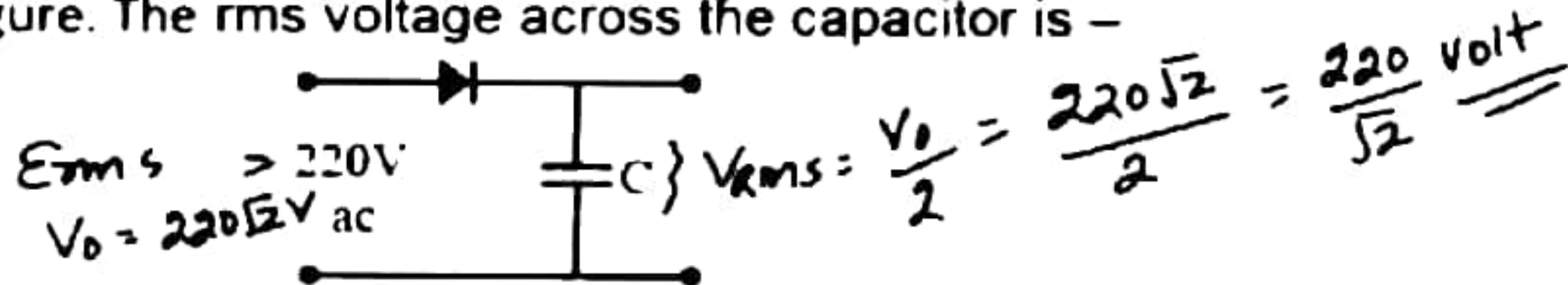11.

A diode is connected to 220 V (rms) ac in series with a capacitor as shown in figure. The rms voltage across the capacitor is –




- (A) 220 V      (B) 110 V      (C) 311.1 V

~~(D)~~  $\frac{220}{\sqrt{2}} \text{ V}$

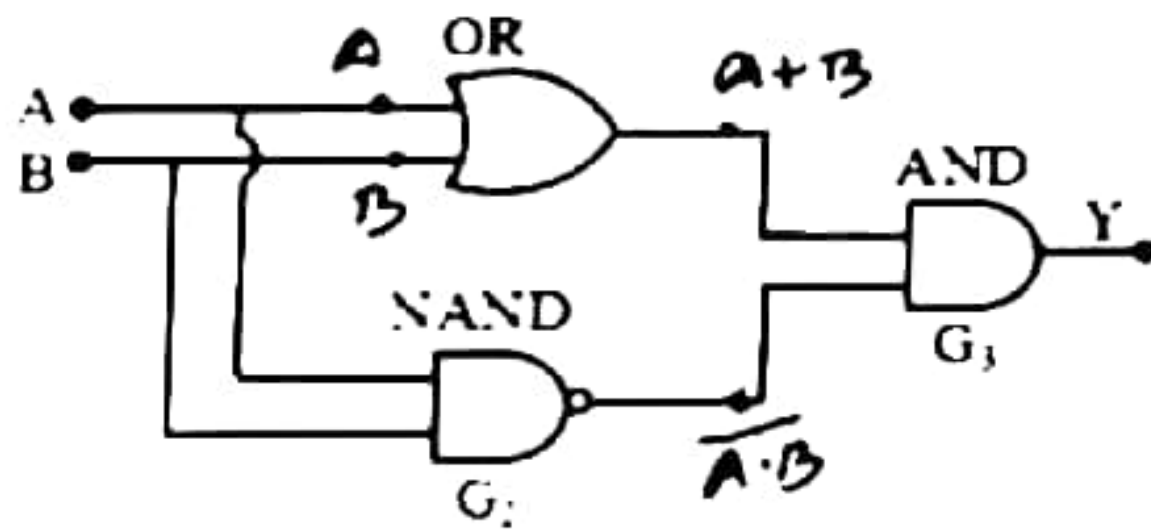12.

The following configuration of gate is equivalent to-



- (A) NAND      ~~(B) XOR~~      (C) OR      (D) None of these





$$\begin{aligned}
 Y &= (A+B) \cdot (\overline{A \cdot B}) \\
 &= (A+B) \cdot (\overline{A} + \overline{B}) \\
 &= A\overline{A} + B\overline{A} + A\overline{B} + B\overline{B} \\
 &= 0\overline{A} + A\overline{B} + A\overline{B} + 0 \\
 &= \underline{A\overline{B} + A\overline{B}} \quad \underline{\underline{(XOR)}}
 \end{aligned}$$

13.

A combination of logic gates has the truth table below

P	Q	Z
0	0	0
0	1	1
1	0	1
1	1	1

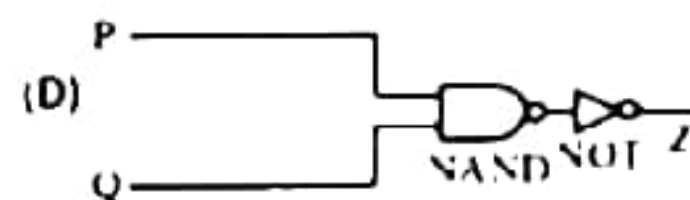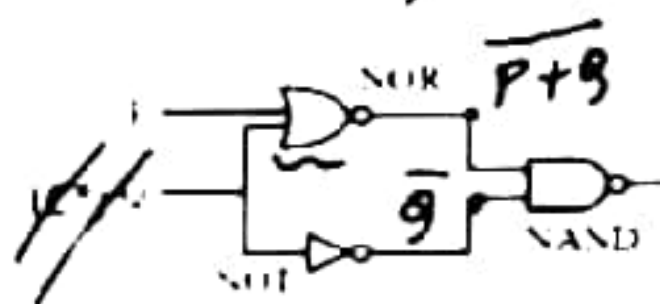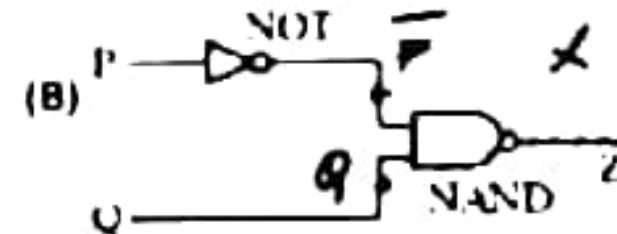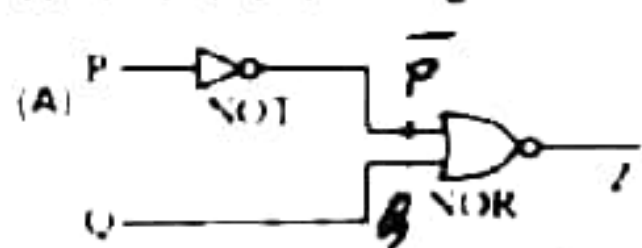Which of the following combinations has this truth table?



Sol<sup>n</sup> a)  $Z = \overline{P+Q}$   
 $= \overline{P} \cdot \overline{Q}$  X  
 $= P\overline{Q}$

P	Q	$\overline{P} \cdot \overline{Q}$	$P\overline{Q}$
0	0	1	0
0	1	0	0
1	0	1	1
1	1	0	0

b)  $Z = \overline{P \cdot Q}$  X  
 $= \overline{P} + \overline{Q}$   
 $= P + \overline{Q}$

$P + \overline{Q}$
1
0
1
1

c)  $Z = \overline{(\overline{P+Q}) \cdot \overline{Q}}$

$Z = \overline{P+Q} + \overline{Q}$

$Z = P+Q+Q$

$Z = P+Q$

$Z = 0$


1  
1  
1



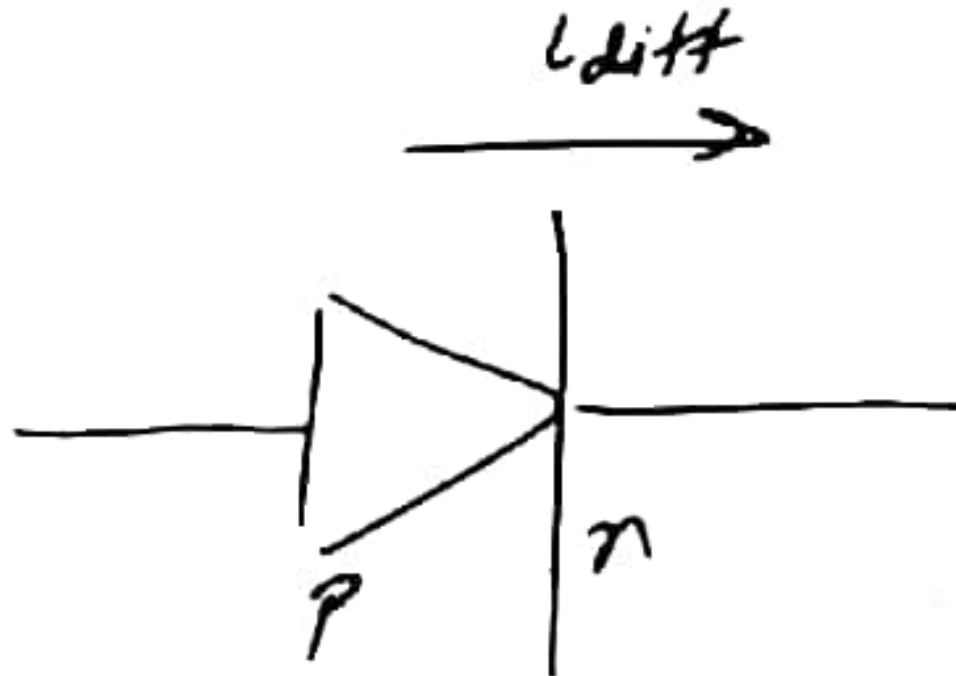14.

In a p-n junction diode the direction of diffusion current is from -

- ☒ (A) p-region to n-region
- (B) n-region to p-region
- (C) n-region to p-region when forward biased and vice-versa when reverse biased
- (D) p-region to n-region when forward biased and vice-versa when reverse biased







15.

Choose only false statement from the following -

- (A) In conductors the valence and conduction band overlap *Correct*
- (B) Substance with energy gap of the order of 10 eV are insulators *Correct*
- ☒ (C) The resistivity of a semi conductor increase with increase in temperature *Incorrect*
- (D) The conductivity of semiconductor increase with increase in temperature *Correct*

16.

Match column 1 with column 2

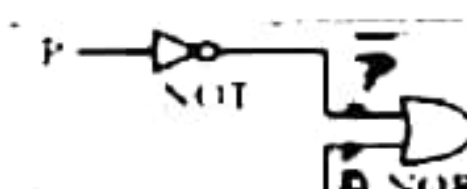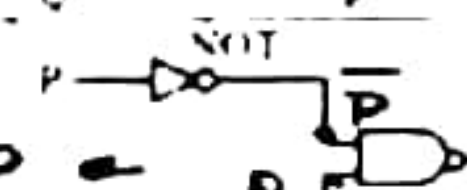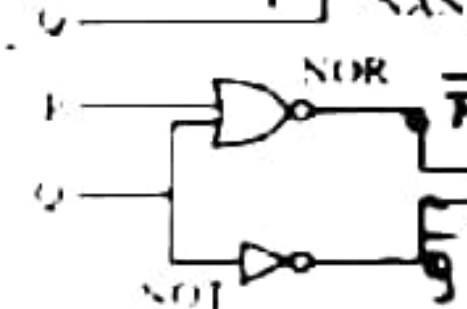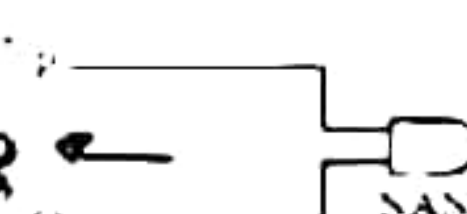Column I	Column II
(A) 	(P) $Z = P + \bar{Q}$
(B) 	(Q) $Z = P + Q$
(C) 	(R) $Z = P \cdot Q$
(D) 	(S) $Z = (P \cdot Q)$

(A) A → R; B → P; C → Q; D → S

(B) A → S; B → P; C → Q; D → R

(C) A → S; B → P; C → R; D → Q

(D) A → P; B → S; C → Q; D → R

17.


How many minimum "NOR" gates are required to make one "NAND" gate -

(A) 1

(B) 2

(C) 3

~~(D) 4~~

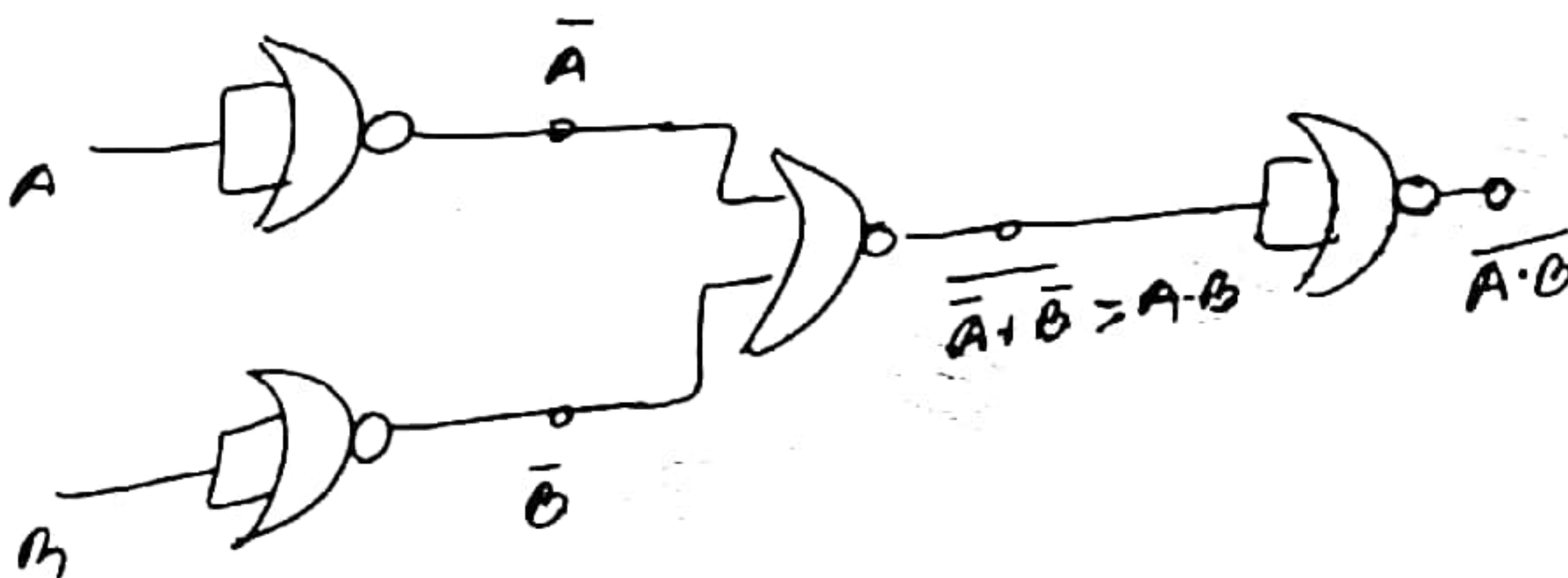




18.

Which statement is correct for p-type semiconductor -

- (A) the number of electrons in conduction band is more than the number of holes in valence band at room temperature
- ☒ (B) the number of holes in valence band is more than the number of electrons in conduction band at room temperature
- (C) there are no holes and electrons at room temperature
- (D) number of holes and electrons is equal in valence and conduction band

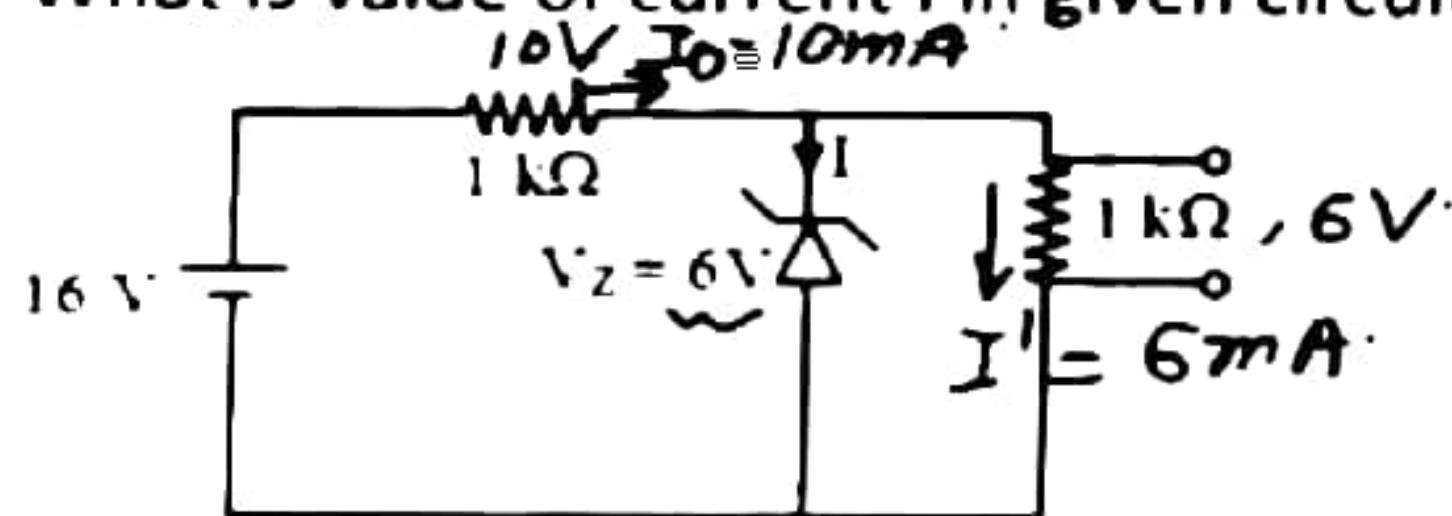19.

What is value of current  $I$  in given circuit. -



- (A) 6 mA
- ☒ (B) 4 mA
- (C) 10 mA
- (D) zero






$$I_0 = I + I'$$

$$10\text{ mA} = I + 6\text{ mA}$$

$$I = \underline{4\text{ mA}}$$

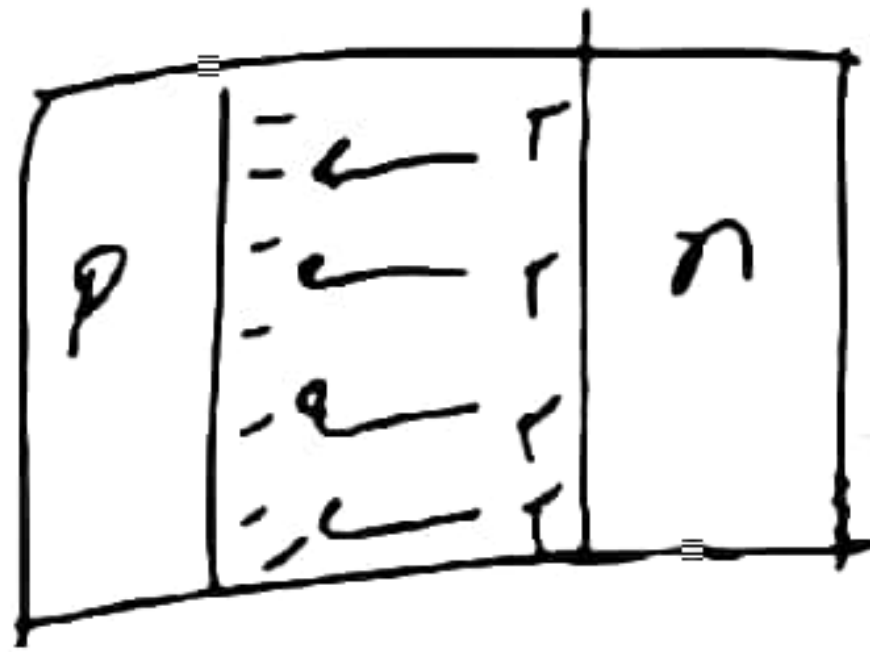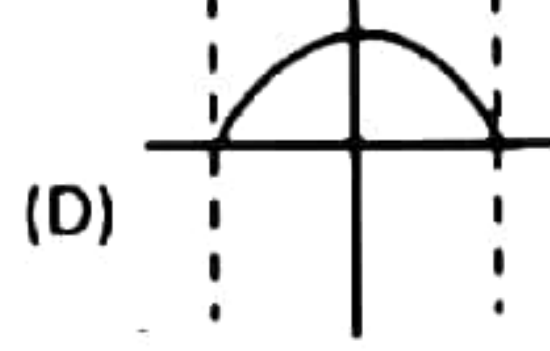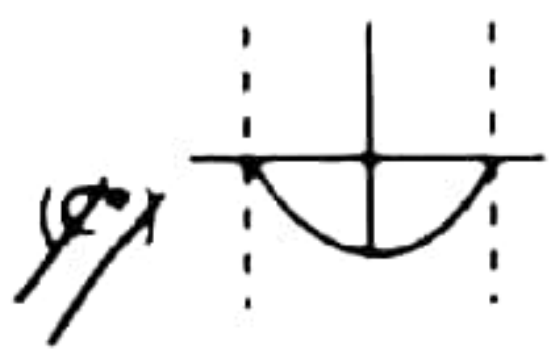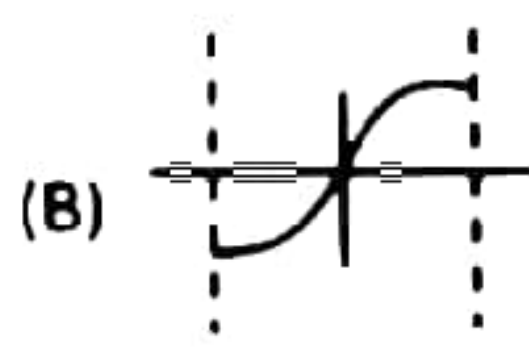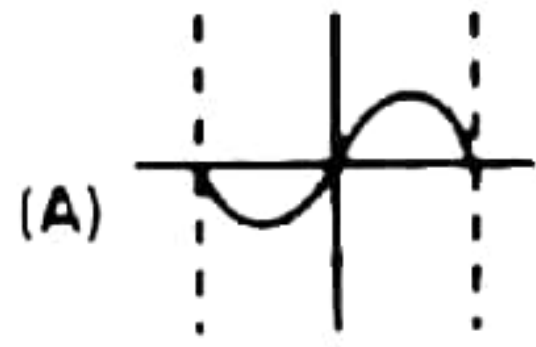20.

Which graph shows correct variation of electric field across depletion layer of p-n junction -



21.

The maxwell's equation :

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 \left( I + \epsilon_0 \frac{d\phi_E}{dt} \right) \text{ is a statement of -}$$

(A) Faraday's law of induction

~~(B) Modified Ampere's law~~

(C) Gauss's law of electricity

(D) Gauss's law of magnetism



22.

The relation between electric field  $E$  and magnetic field  $H$  in an electromagnetic wave is-

- (A)  $E = H$       (B)  $E = \frac{\mu_0}{\epsilon_0} H$       ~~(C)  $E = \sqrt{\frac{\mu_0}{\epsilon_0}} H$~~       (D)  $E = \sqrt{\frac{\epsilon_0}{\mu_0}} H$

$$\frac{E}{B} = c$$

$$E = B \times \frac{1}{\sqrt{\mu_0 \epsilon_0}}$$

$$H = \frac{B}{\mu_0}$$

$$E = \frac{\mu_0 H}{\sqrt{\mu_0 \epsilon_0}}$$

$$E = \sqrt{\frac{\mu_0}{\epsilon_0}} \times H$$

23.

The relation between electric field  $E$  and magnetic field induction  $B$  in an electromagnetic waves-

- (A)  $E = \sqrt{\frac{\mu_0}{\epsilon_0}} B$       ~~(B)  $E = cB$~~       (C)  $E = \frac{B}{c}$       (D)  $E = \frac{B}{c^2}$

24.

An electromagnetic wave going through vacuum is described by-

$$E = E_0 \sin(kx - \omega t)$$

$$B = B_0 \sin(kx - \omega t)$$

- (A)  $E_0 B_0 = \omega k$       (B)  $E_0 \omega = B_0 k$       ~~(C)  $E_0 k = B_0 \omega$~~       (D) none of these

$$\frac{E_0}{B_0} = v = \frac{\omega}{k}$$

$$E_0 k = \omega B_0$$

25.

A plane E M wave of frequency 25 MHz travels in free space in x direction. At a particular point in space and time  $E = 6.3 \text{ V/m}$  then B at that point is -

- (A)  $2.1 \times 10^{-8} \text{ T}$       ~~(B)  $2.1 \times 10^{-8} \text{ T}$~~   
 (C)  $2.1 \text{ T}$       (D)  $2.1 \times 10^{-8} \text{ T}$

$$\frac{E}{B} = c$$

$$\frac{6.3}{3 \times 10^8} = B$$

$$\vec{B} = 2.1 \times 10^{-8} \text{ T} \hat{k}$$

26.

The average value of electric energy density in an electromagnetic wave is ( $E_0$  is peak value) -

- (A)  $\frac{1}{2} \epsilon_0 E_0^2$       (B)  $\frac{E_0^2}{2\epsilon_0}$       (C)  $\epsilon_0 E_0^2$       ~~(D)  $\frac{1}{4} \epsilon_0 E_0^2$~~

$$\overline{u} = \frac{1}{2} \epsilon_0 \overline{E^2}$$


$$\overline{u} = \frac{1}{4} \epsilon_0 E_0^2$$



27.

A lamp radiates power  $P_0$  uniformly in all directions, the amplitude of electric field strength  $E_0$  at a distance  $r$  from it is-

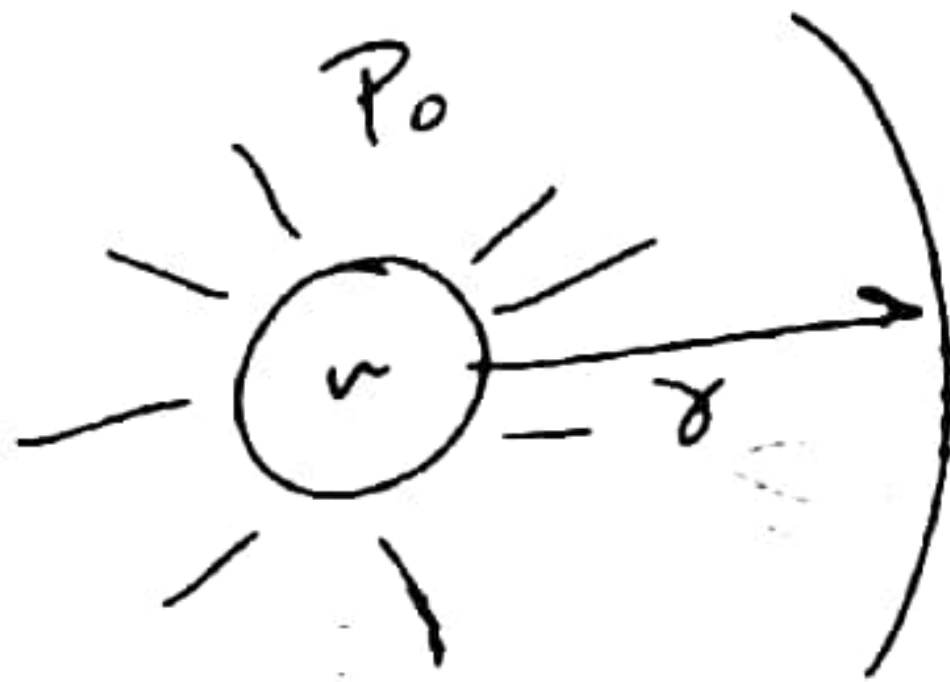- (A)  $E_0 = \frac{P_0}{2\pi\epsilon_0 cr^2}$       ~~(B)~~  $E_0 = \sqrt{\frac{P_0}{2\pi\epsilon_0 cr^2}}$   
 (C)  $E_0 = \sqrt{\frac{P_0}{4\pi\epsilon_0 cr^2}}$       (D)  $E_0 = \sqrt{\frac{P_0}{8\pi\epsilon_0 cr}}$



$$I = \frac{P_0}{4\pi r^2} = \bar{u} c$$


$$\frac{P_0}{4\pi r^2} = \frac{1}{2} \epsilon_0 E_0^2 \cdot c$$

$$E_0 = \sqrt{\frac{P_0}{2\pi r^2 c \epsilon_0}}$$

28.

A parallel plate capacitor consists of two circular plates each of radius 2 cm, separated by a distance of 0.1 mm. If voltage across the plates is varying at the rate of  $5 \times 10^{13}$  V/s, then the value of displacement current is-

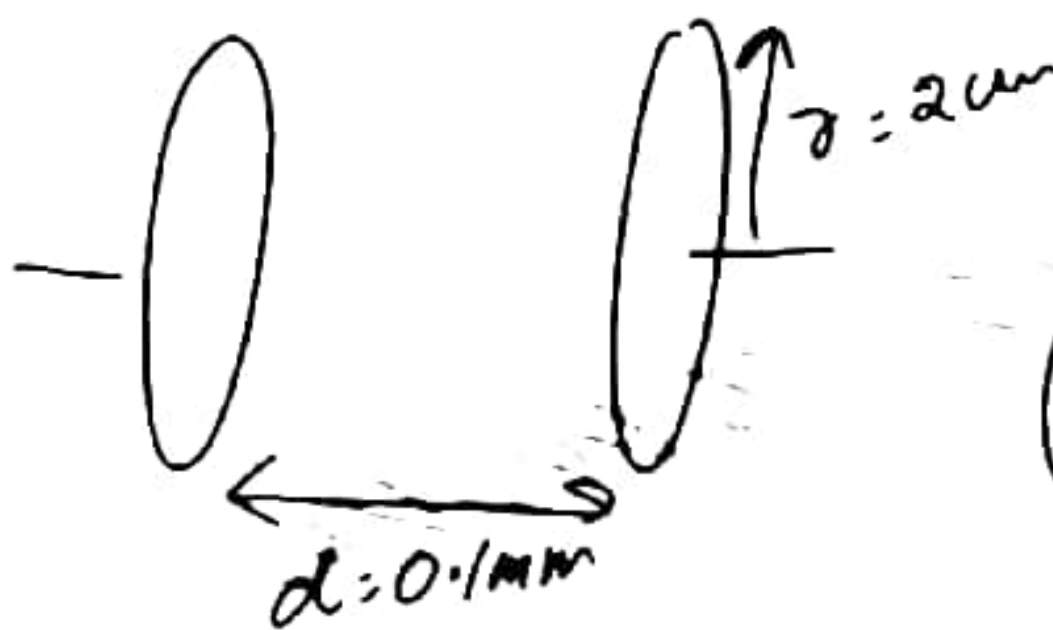- (A) 5.50 A      (B)  $5.56 \times 10^2$  A  
~~(C)~~  $5.56 \times 10^3$  A      (D)  $2.28 \times 10^4$  A



$$\frac{dV}{dt} = 5 \times 10^{13} \text{ V/s}$$

$$q = CV$$

$$\frac{dq}{dt} = C \frac{dV}{dt}$$

$$i = \frac{4\pi\epsilon_0 r^2}{4d} \frac{dV}{dt}$$

$$i = \frac{1 \times 4 \times 10^{-4} \times 5 \times 10^{13}}{9 \times 10^9 \times 4 \times 10^{-4}}$$

$$i = 5.56 \times 10^3 \text{ A}$$

29.

In an electromagnetic wave-

- (A) Power is transmitted along the magnetic field
- (B) power is transmitted along the electric field
- (C) power is equally transferred along the electric and magnetic fields
- ~~(D)~~ power is transmitted in a direction perpendicular to both the fields

30.

For any E.M. wave if  $E = 100 \text{ V/m}$  and  $B = 3.33 \times 10^{-7} \text{ T}$ . Then the rate of energy flow per unit area is-

- (A)  $3.33 \times 10^{-5} \text{ J/m}^2$
- ~~(B)~~  $26.5 \text{ VA/m}^2$
- (C)  $3 \times 10^8 \text{ J/m}^2$
- (D) None of these

$$\begin{aligned} \text{Rate of energy flow/Area} &= \text{Intensity} = |\vec{S}| = \frac{|\vec{E} \times \vec{B}|}{\mu_0} \\ &= \frac{EB}{\mu_0} \\ &= \frac{100 \times 3.33 \times 10^{-7}}{4\pi \times 10^{-7}} \\ &= \frac{333}{4\pi} = 26.5 \frac{\text{W}}{\text{m}^2} = 26.5 \frac{\text{V} \cdot \text{A}}{\text{m}^2} \end{aligned}$$



31.

In an electromagnetic wave, the amplitude of electric field is 10 V/m. The frequency of wave is  $5 \times 10^{14}$  Hz, the wave is propagating along z-axis, then total average energy density of E.M. wave is -

- (A)  $2.21 \times 10^{-10} \text{ J/m}^3$       ~~(B\*)~~  $4.42 \times 10^{-10} \text{ J/m}^3$   
 (C)  $1.11 \times 10^{-10} \text{ J/m}^3$       (D) None

Sol<sup>n</sup>       $E_0 = 10 \text{ V/m}$

$$\begin{aligned} \bar{u} &= \frac{1}{2} \epsilon_0 E_0^2 \\ &= \frac{1}{2} \times 8.85 \times 10^{-12} \times 100 \\ &= 4.42 \times 10^{-10} \text{ J/m}^3 \end{aligned}$$

32.

The resonance frequency of the tank circuit of an oscillator when  $L = \frac{10}{\pi^2} \text{ mH}$  and  $C = 0.04 \mu \text{ F}$  are connected in parallel is:

- (A) 250 kHz      ~~(B\*)~~ 25 kHz      (C) 2.5 kHz      (D) 25 MHz

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\begin{aligned} &= \frac{1}{2\pi\sqrt{\frac{10 \times 10^{-3}}{\pi^2} \times 4 \times 10^{-8}}} \\ &= \frac{1}{2\sqrt{4 \times 10^{-10}}} = \frac{1}{4 \times 10^{-5}} \text{ Hz} \\ &= \frac{100}{4} \text{ kHz} \\ &= \underline{25 \text{ kHz}} \end{aligned}$$


33.

Semiconductor is damaged by the strong current due to

- (A) Lack of free electron
- ~~(B\*)~~ (B) Excess of electrons
- (C) Excess of proton
- (D) None of these

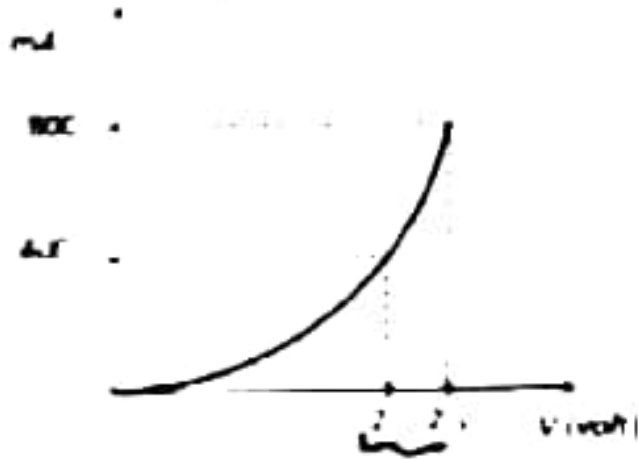34.

The  $I-V$  characteristic of a  $P-N$  junction diode is shown below. The approximate dynamic resistance of the  $P-N$  junction when a forward bias of 2 volt is applied



- (A)  $1 \Omega$
- ~~(B\*)~~ (B)  $0.25 \Omega$
- (C)  $0.5 \Omega$
- (D)  $5 \Omega$

$$R_{\text{dynamic}} = \frac{\Delta V}{\Delta I} = \frac{0.1 \text{ Volt}}{400 \text{ mA}} = \frac{1}{4} \Omega = 0.25 \Omega$$

35.


Zener breakdown in a semi-conductor diode occurs when

- (A) Forward current exceeds certain value
- (B) Reverse bias exceeds certain value
- (C) Forward bias exceeds certain value
- ~~(D\*)~~ (D) Potential barrier is reduced to zero




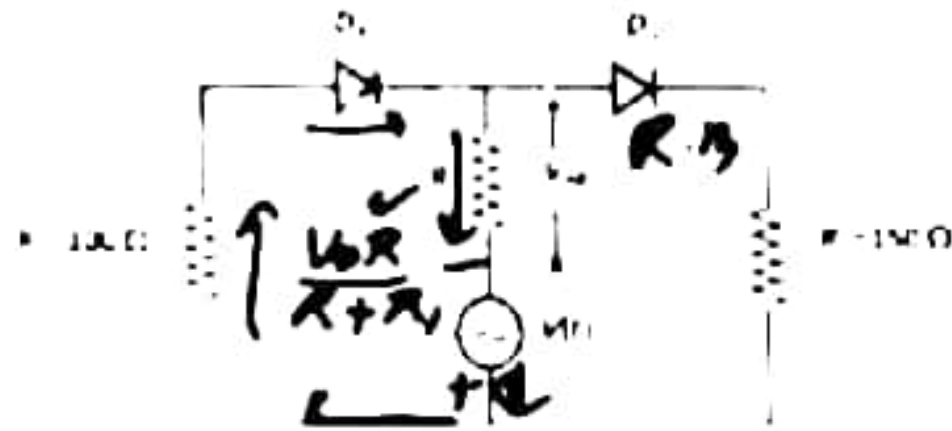36.

In the circuit given below,  $V(t)$  is the sinusoidal voltage source, voltage drop  $V_{AR}(t)$  across the resistance  $R$  is




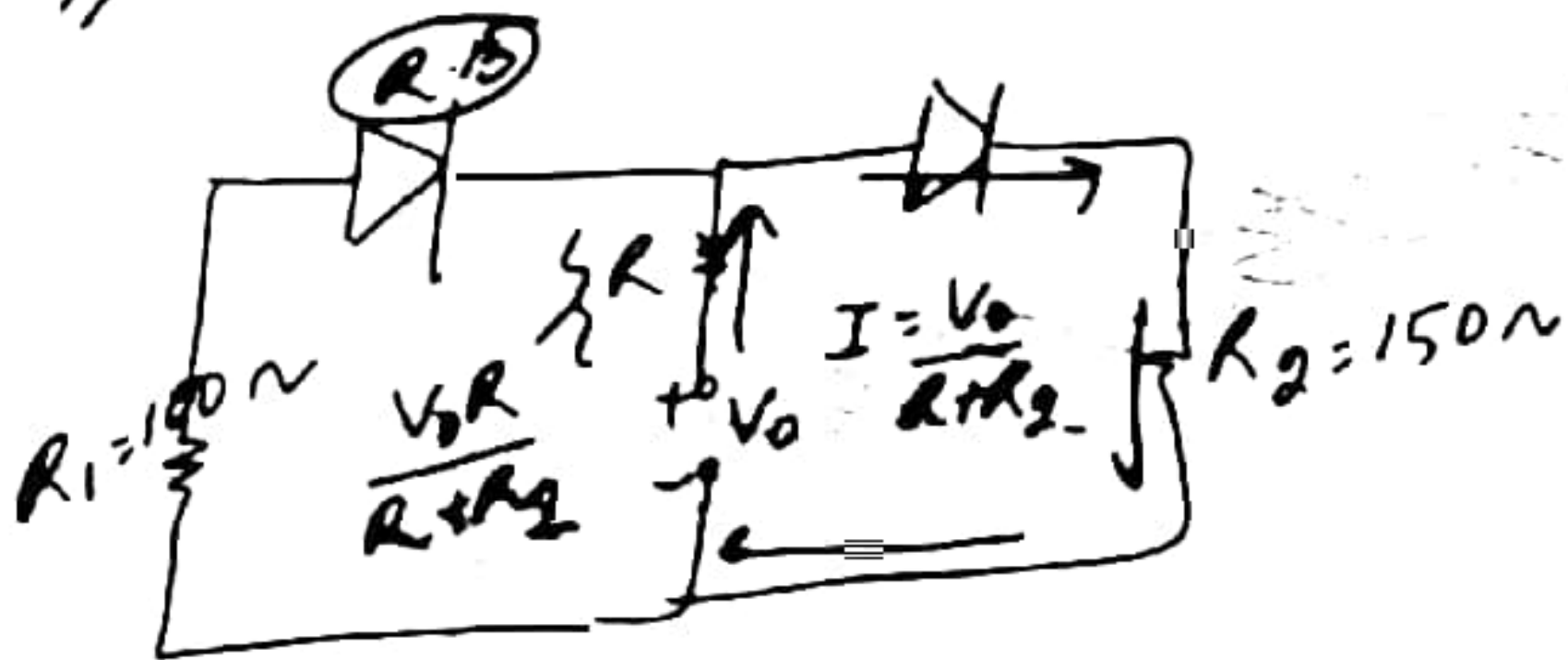- (A) Is half wave rectified ☒   
 (B) Is full wave rectified ☒   
 (C) Has the same peak value in the positive and negative half cycles ☒   
 (D) Has different peak values during positive and negative half cycle ☒



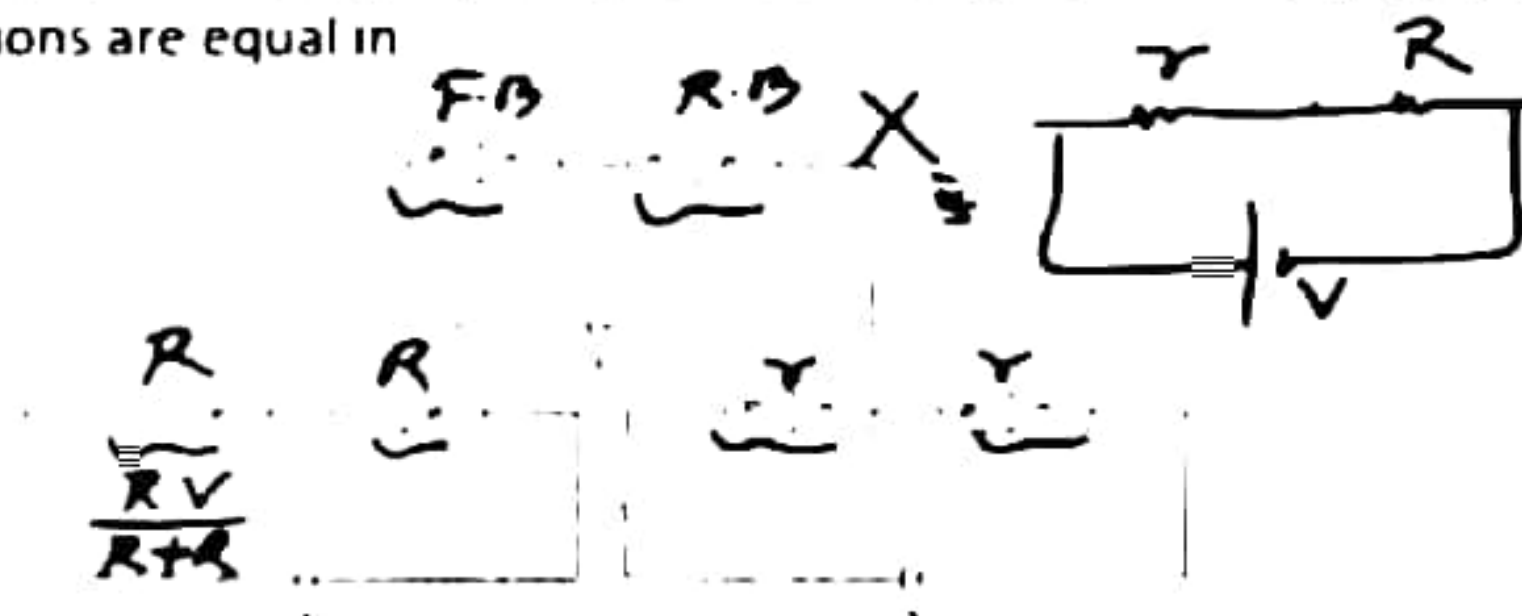37.

Two identical  $p-n$  junctions are connected in series in three different ways as shown below to a battery. The potential drop across the  $p-n$  junctions are equal in




- (A) Circuits 2 and 3 ☒   
 (B) Circuits 1 and 2 ☒   
 (C) Circuits 1 and 3 ☒   
 (D) None of the circuit ☒

$$R_{FB} = r$$

$$R_{AB} = R$$

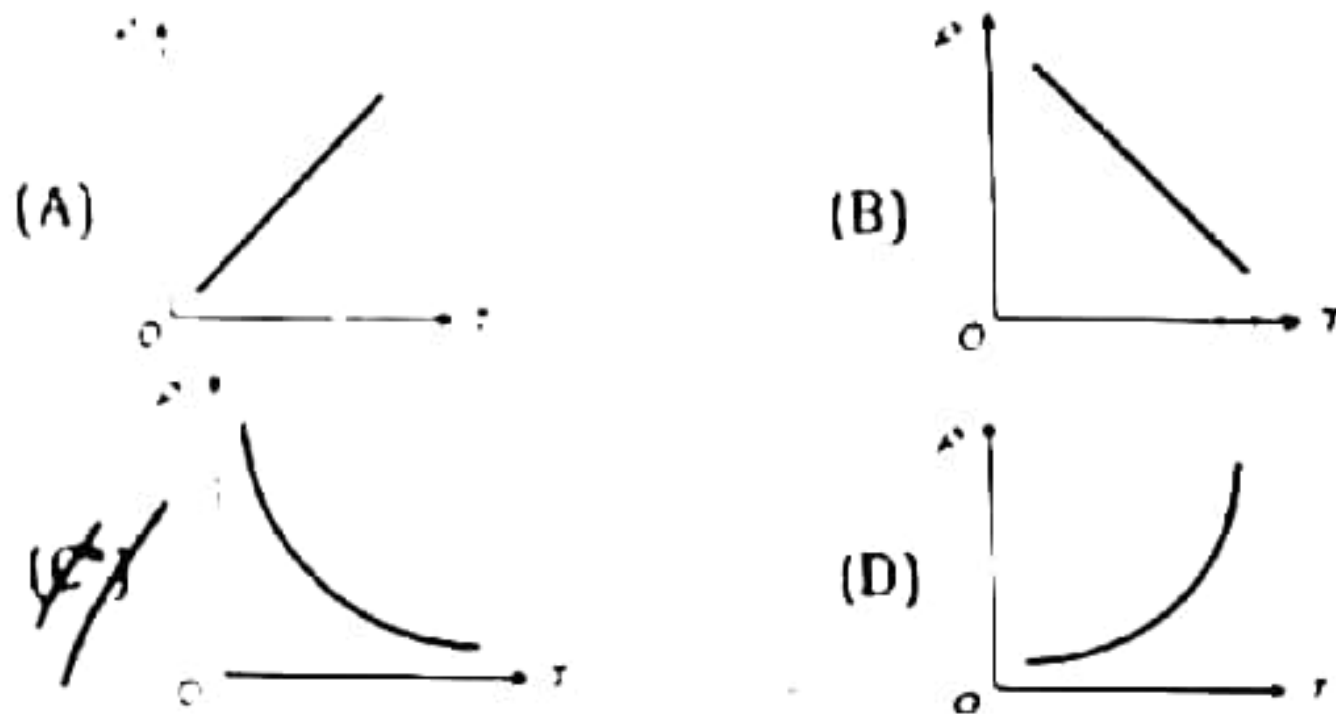38.

The temperature ( $T$ ) dependence on resistivity ( $\rho$ ) of a semiconductor is represented by



39.

For a common emitter amplifier, the audio signal voltage across the collector resistance  $2\text{ k}\Omega$  is  $2\text{ V}$ . If the current amplification factor of the transistor is  $220$ , and the base resistance is  $1.5\text{ k}\Omega$ , the input signal voltage and base current are

- (A)  $0.1\text{ V}$  and  $1\text{ }\mu\text{A}$   
(C)  $1.015\text{ V}$  and  $1\text{ A}$

- (B)  $0.15\text{ V}$  and  $10\text{ }\mu\text{A}$   
(D)  $0.0075\text{ V}$  and  $5\text{ }\mu\text{A}$

$$\begin{aligned} V_o &= 2\text{ V} \\ R_c &= 2\text{ k}\Omega \\ \beta &= 220 \\ R_b &= 1.5\text{ k}\Omega \\ V_i &=? \\ I_b &=? \end{aligned}$$

$$V_o = \beta \times R_c \times I_b$$

$$\frac{V_o}{V_i} = \beta \times \frac{R_c}{R_b}$$

$$\frac{2}{V_i} = 220 \times \frac{2}{1.5}$$


$$V_i = 0.0075\text{ Volt}$$

$$\begin{aligned} V_o &= I_c R_c \\ 2 &= I_c \times 2\text{ k}\Omega \\ I_c &= 1\text{ mA} \\ \beta &= \frac{I_c}{I_b} \\ I_b &= \frac{1\text{ mA}}{220} \\ &\approx 5\text{ }\mu\text{A} \end{aligned}$$




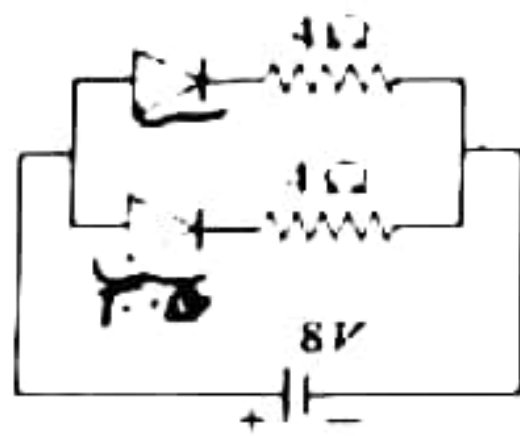40.

Currents flowing in each of the circuits A and B respectively are



(Circuit A)

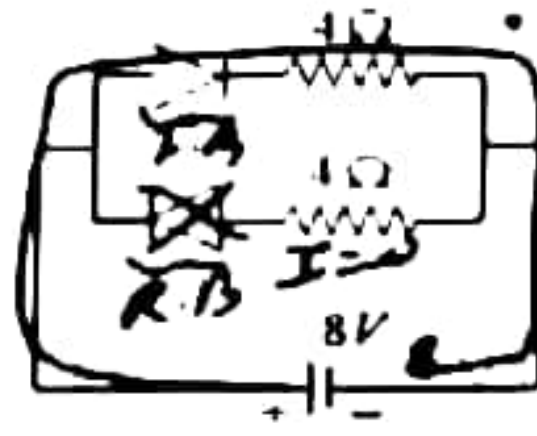

(Circuit B)

(A) 1 A, 2 A

(B) 2 A, 1 A

~~(C) 4 A, 2 A~~

(D) 2 A, 4 A



$$I_A = \frac{8}{2} = 4A$$

41.

For a junction diode the ratio of forward current ( $I_F$ ) and reverse current ( $I_r$ ) is?

[ $e$  = electronic charge,  $V$  = voltage applied across junction,  $k$  = Boltzmann constant,  $T$  = temperature in kelvin]

(A)  $e^{-V/kT}$

(B)  $e^{V/kT}$

(C)  $(e^{-eV/kT} + 1)$


~~(D)~~  $(e^{eV/kT} - 1)$

$$I_F = I_0 (e^{eV/kT} - 1)$$

$$\frac{I_F}{I_r} = e^{eV/kT} - 1$$

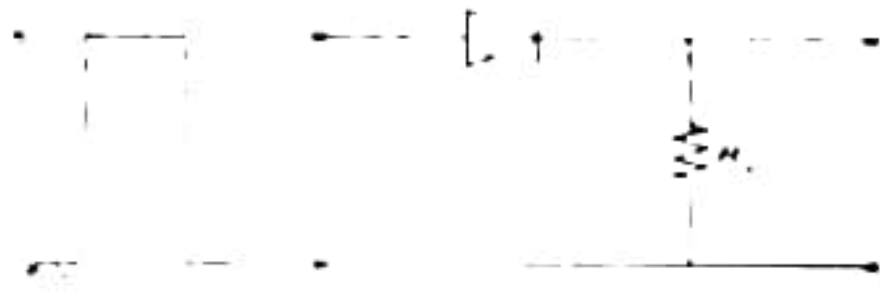42.

If in a p-n junction diode, a square input signal of 10 V is applied as shown





Then the output signal across  $R_L$  will be

(A)

(B)

(C)

~~(D)~~

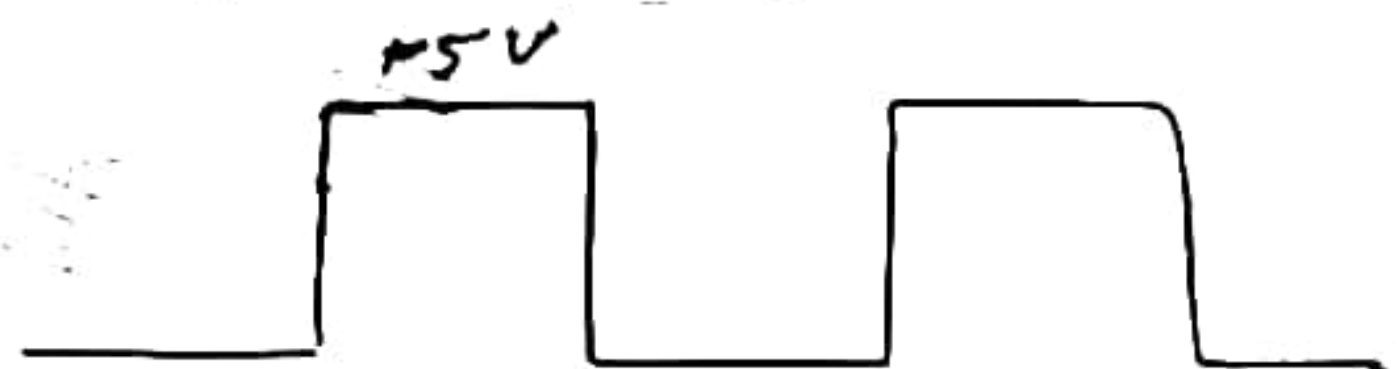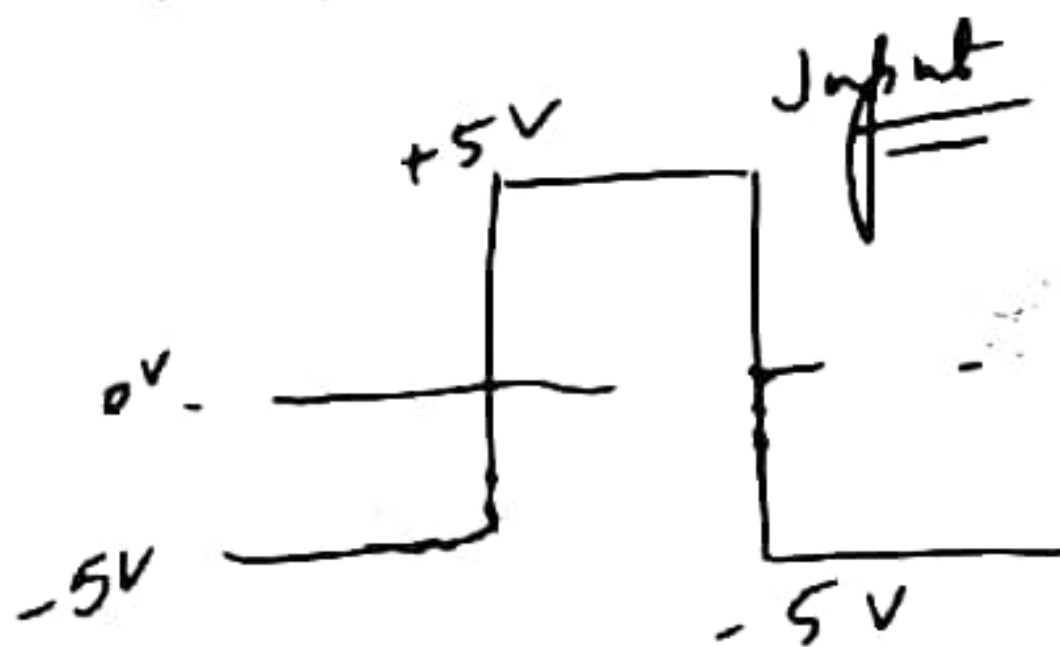

43.

In PN-junction diode the reverse saturation current is  $10^{-5}$  amp at  $27^\circ\text{C}$ . The forward current for a voltage of 0.2 volt is

[ $\exp(7.62) = 2038.6$ ,  $k = 1.4 \times 10^{-23} \text{ J/K}$ ]

(A)  $2037.6 \times 10^{-3} \text{ amp}$

(B)  $203.76 \times 10^{-3} \text{ amp}$

~~(C)~~  $20.376 \times 10^{-3} \text{ amp}$

(D)  $2.0376 \times 10^3 \text{ amp}$

$$I_F = I_0 (e^{eV/kT} - 1)$$

$$I_F = 10^{-5} \left[ e^{\frac{1.6 \times 10^{-19} \times 0.2}{1.4 \times 10^{-23} \times 300}} - 1 \right]$$

$$= 10^{-5} [e^{7.62} - 1]$$


$$= 10^{-5} [2038.6 - 1] = 2037.6 \times 10^{-5} \text{ A}$$

$$= 20.376 \times 10^{-3} \text{ A}$$



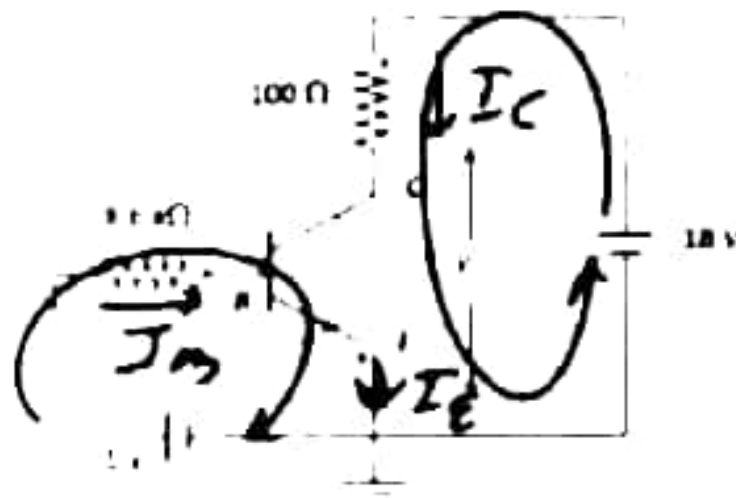44.

For the transistor circuit shown below, if  $\beta = 100$ , voltage drop between emitter and base is  $0.7\text{ V}$  then value of  $V_{CE}$  will be



(A)  $10\text{ V}$

(B)  $5\text{ V}$

~~(C)  $13\text{ V}$~~

(D)  $0\text{ V}$

$$V_{BE} = 0.7\text{ V}$$

$$V - V_{BE} = I_B R_B$$

$$5 - 0.7 = I_B \times 8.6\text{ k}\Omega$$

$$\frac{4.3\text{ V}}{8.6\text{ k}\Omega} = I_B$$

$$I_B = \frac{1}{2}\text{ mA}$$

$$\beta = \frac{I_C}{I_B} \Rightarrow I_C = \frac{1}{2}\text{ mA} \times 100 = 50\text{ mA}$$

$$V - V_{CE} = I_C R_C$$






$$10 - V_{CE} = 50 \times 10^{-3} \times 100$$

$$V_{CE} = (10 - 5)\text{ Volt}$$

$$= 5\text{ Volt}$$

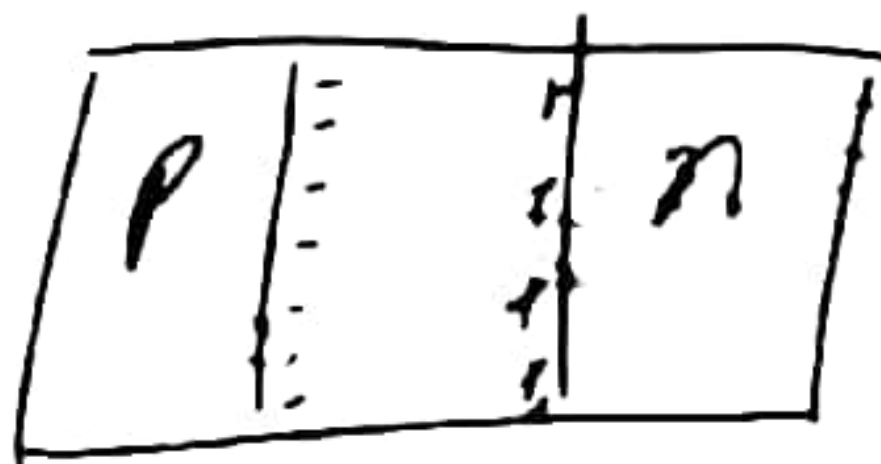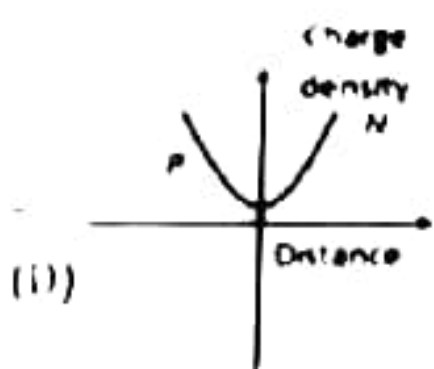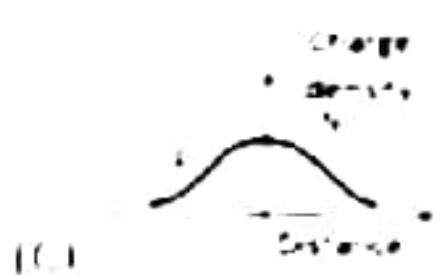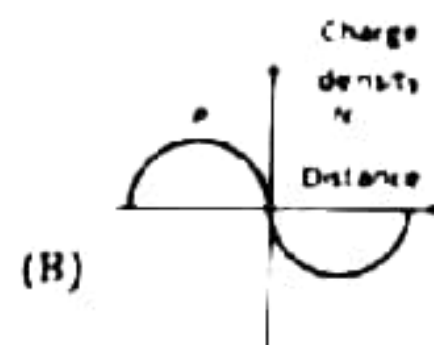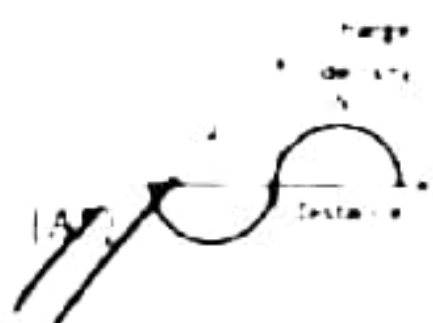45.

The curve between charge density and distance near P-N junction will be



46.

**Statement 1** : Doping concentration is maximum in emitter in transistor. *correct*

**Statement 2** : Maximum number of electrons flows from emitter to base in n-p-n *correct* transistor.

(A) Both Statement-1 and Statement-2 are true, and Statement-2 is the correct explanation of Statement-1.


☒ (B) Both Statement-1 and Statement-2 are true but Statement-2 is not the correct explanation of Statement-1.

(C) Statement-1 is true but Statement-2 is false.

(D) Statement-1 is false but Statement-2 is true.

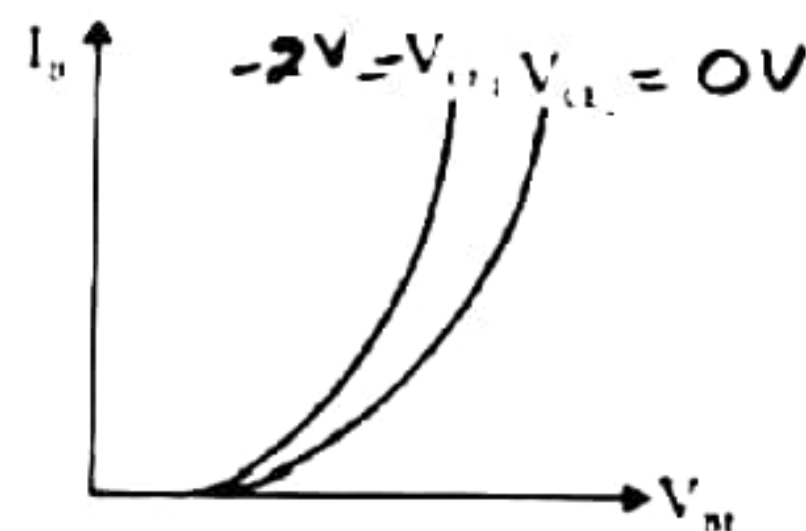47.

Input characteristics are shown for CE configuration of n-p-n transistor for different output voltages. Here



(A)  $V_{CE1} > V_{CE2}$

(B)  $V_{CE1} = V_{CE2}$

☒ (C)  $V_{CE1} < V_{CE2}$

(D) None of these


$$V_{CE1} < V_{CE2}$$

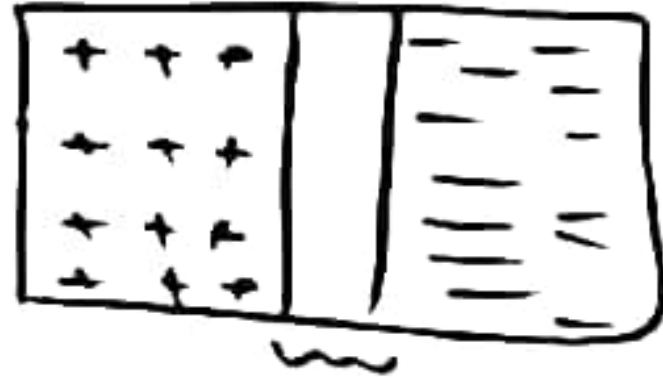48.




Zener diode has both p and n-ends heavily doped so that –

- ✓(A\*) it has small thickness of depletion region
- (B) it has large thickness of depletion region due to large recombination
- (C) it has large reverse bias voltage
- (D) it has weak reverse current when reverse biased



49.

In given figure

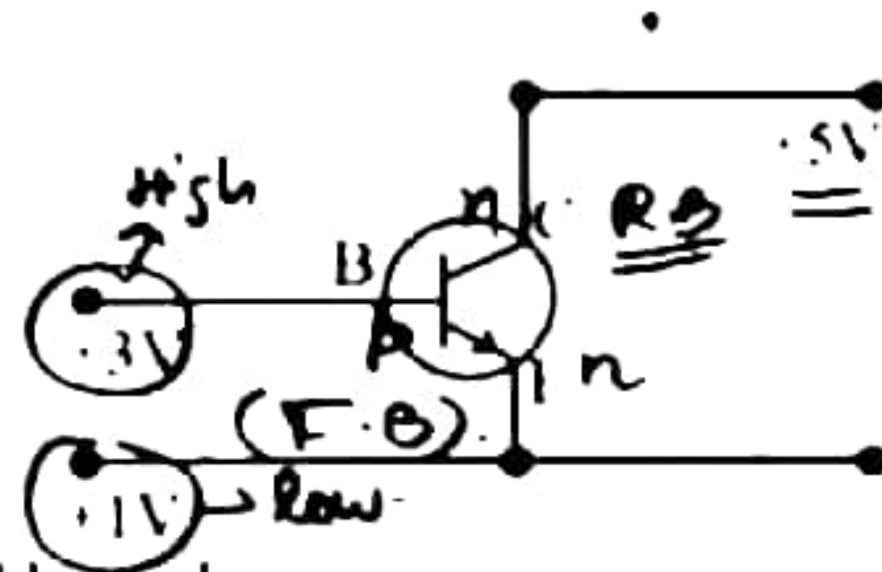

- ✓ (A) emitter is forward biased  
 (B) collector is forward biased ✓  
 (C) emitter is reverse biased ✗  
 (D) emitter and collector both are reverse biased ✓

50.

A condenser is charged using a constant current. The ratio of the magnetic fields at a distance of  $R/2$  and  $R$  from the axis is ( $R$  is the radius of plate)

- A) 1:1      B) 2:1      ✓ C) 1:2      D) 1:4

sol<sup>n</sup>

